

Basic Electrical / Electronic Circuit Components



Circuit Components

Passive Components: Resistors, Capacitors, Inductors, transformer etc.



Active Components: Power sources (voltage/current),
Transistors (BJT/ MOSFET),
Generators etc

(Ideal Voltage Sources)

DC Voltage Source

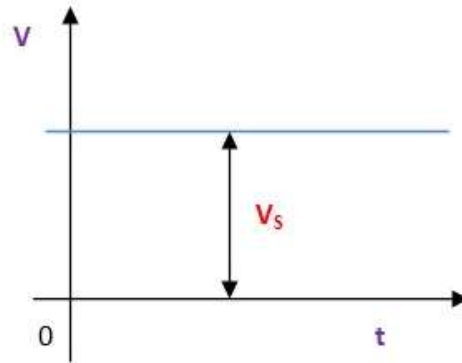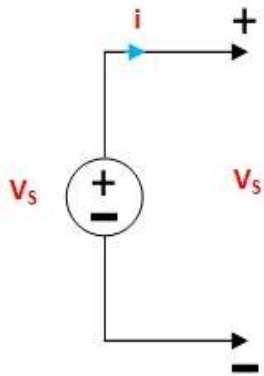

Alternating Voltage Source

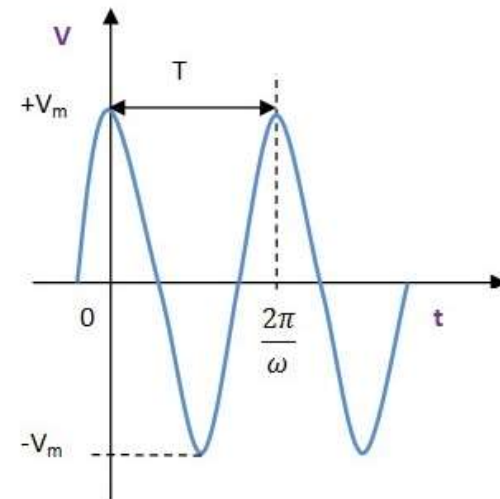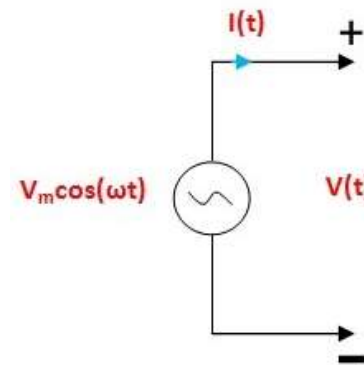

Sources Types (DC/AC)

A. Independent

1. Voltage


2. Current




Independent
Current Source



Dependent
Current Source

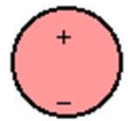

Independent
Voltage Source

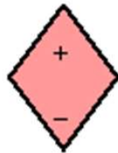

Dependent
Voltage Source


B. Dependent

1. Voltage dependent Voltage Source, $v(v_x)$


2. Current dependent Voltage Source, $v(i_x)$

3. Voltage dependent Current Source, $i(v_x)$


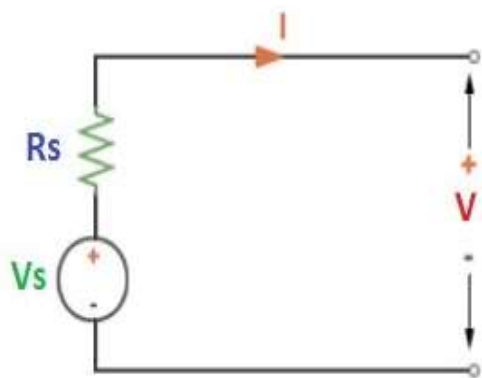
4. Current dependent Current Source, $i(i_x)$




Practical Voltage Source

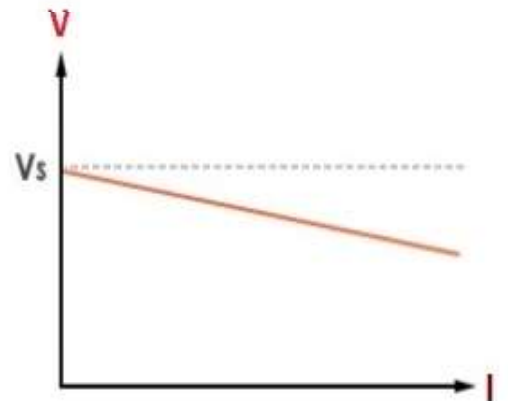


Practical Voltage Source Graph

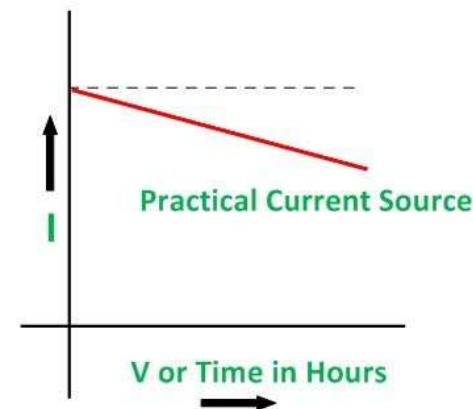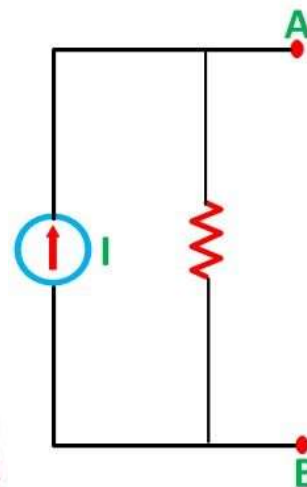


Linear Time Invariant Passive Elements

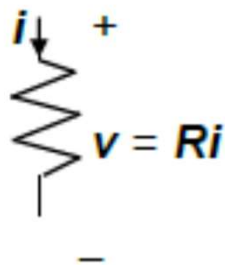

Linear Resistor

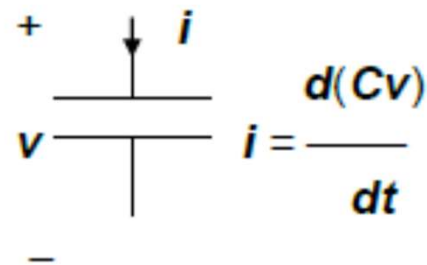

Linear Capacitor

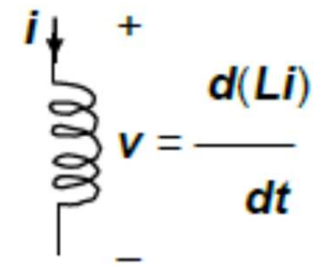

Linear Inductor

For linear time-invariant capacitors and inductors, $i = C(dv/dt)$ and $v = L(di/dt)$ respectively.

Steady State and Transient Behaviour

Capacitor

A capacitor stores energy in the form of an electric field

Current-voltage relationship $i = C \frac{dv}{dt}, \quad v = \frac{1}{C} \int i dt$

In DC the capacitor acts as an open circuit


The capacitance C represents the efficiency of storing charge.

The unit of capacitance is the Farad (F). 1 Farad=1Coulomb/1Vol

Typical capacitor values are in the mF (10^{-3} F) to pF (10^{-12} F)

The energy stored in a capacitor is $E = \frac{1}{2} C v^2$

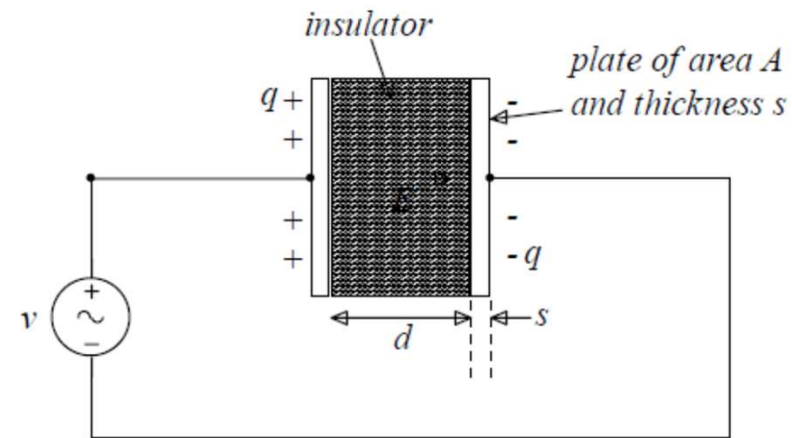Large capacitors should always be stored with shorted leads.



$$\boxed{i = C \frac{dv}{dt}} \quad (1)$$

Integrating Eq.1

$$\begin{aligned} \int_{-\infty}^t i dt &= \int_{-\infty}^t C \frac{dv}{dt} dt \\ v &= \frac{1}{C} \int_{-\infty}^t i dt \\ &= \frac{1}{C} \int_0^t i dt + v(0) \end{aligned}$$

The constant of integration $v(0)$ represents the voltage of the capacitor at time $t=0$.

The presence of the constant of integration $v(0)$ is the reason for the memory properties of the capacitor.

Inductor


A inductor stores energy in a magnetic field

Current-voltage relationship $\boxed{v = L \frac{di}{dt}, \quad i = \frac{1}{L} \int v dt}$

The energy stored in an inductor is $E = \frac{1}{2} Li^2$

In DC the inductor behaves like a short circuit

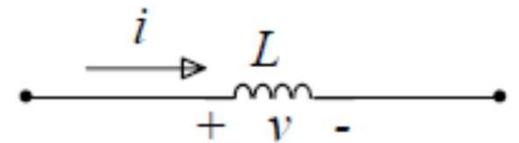The inductance L represents the efficiency of storing magnetic flux.



$$\boxed{v = L \frac{di}{dt}} \quad (2)$$

On integrating Eq. 2

$$\int_{-\infty}^t v dt = \int_{-\infty}^t L \frac{di}{dt} dt$$

$$i = \frac{1}{L} \int_{-\infty}^t v dt$$

$$= \frac{1}{L} \int_0^t v dt + i(0)$$

The constant $i(0)$ represents the current through the inductor at time $t=0$. (Note that we have also assumed that the current at $t = -\infty$ was zero.)

Q. 1.

Calculate the energy stored in the capacitor of the circuit to the right under DC conditions.

